Ladder Logic Example: Motor Start/Stop Circuit with Seal−In
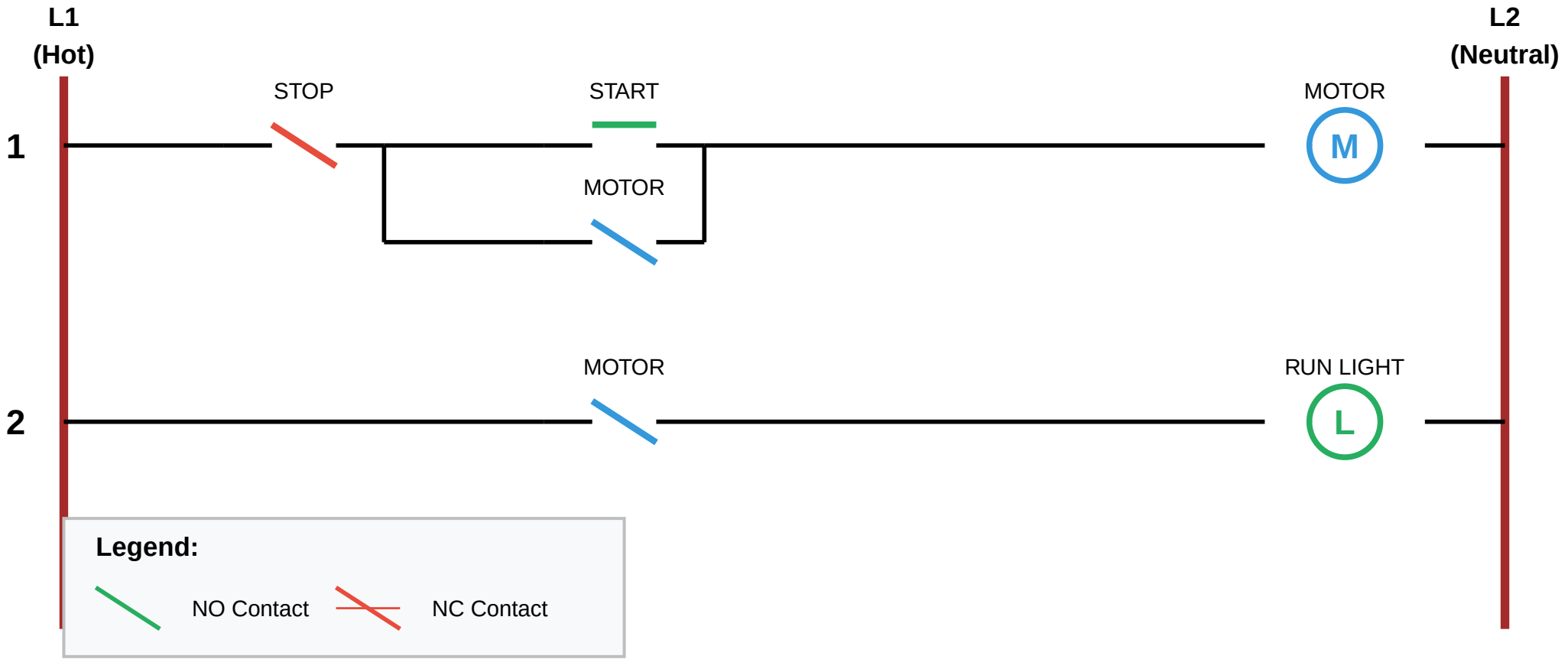
Classic 3−wire control circuit implemented in PLC ladder logic